
# Induction and Inductance Chapter 30
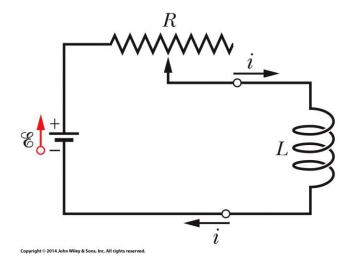
# **30-5 Self-Induction**

When current flow in an inductor a process called self induction happen. This process (see Figure), and the emf that appears is called a self-induced emf. It obeys Faraday's law of induction just as other induced emfs do. For any inductor of inductance L and number of turns N and current i,



$$N\Phi_{B}=Li.$$

# **30-5 Self-Induction**

Faraday's law tells us that


$$\Xi_L = -\frac{d\left(N\Phi_B\right)}{dt}.$$

By combining these equations, we can write

$$E_L = -L \frac{di}{dt}$$
 (self-induced emf).

An induced emf  $\Xi_L$  appears in any coil in which the current is changing.

Note: Thus, in any inductor (such as a coil, a solenoid, or a toroid) a self-induced emf appears whenever the current changes with time. The magnitude of the current has no influence on the magnitude of the induced emf; only the rate of change of the current counts.

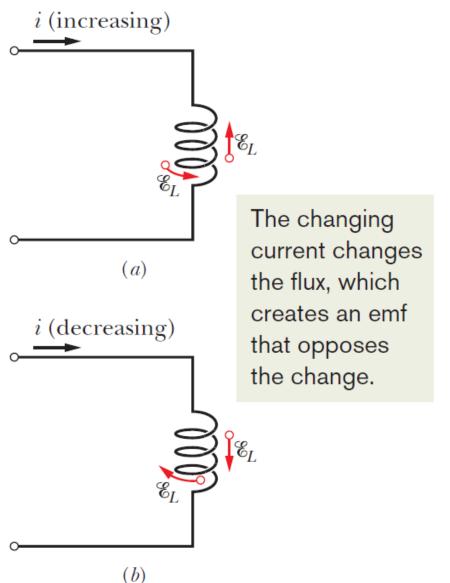

**Figure 30-14** (a) The current i is increasing, and the self-induced emf  $\mathcal{E}_L$  appears along the coil in a direction such that it opposes the increase. The arrow representing  $\mathcal{E}_L$  can be drawn along a turn of the coil or alongside the coil. Both are shown. (b) The current i is decreasing, and the self-induced emf appears in a direction such that it opposes the decrease.



### Checkpoint 5

The figure shows an emf  $\mathscr{E}_L$  induced in a coil. Which of the following can describe the current through the coil:



(a) constant and rightward, (b) constant and leftward,

(c) increasing and rightward, (d) decreasing and rightward, (e) increasing and leftward, (f) decreasing and leftward?

#### d and e

# **30-6 RL Circuits**

If a constant emf  $\Xi$  is introduced into a single-loop circuit containing a resistance R and an inductance L, the current rises to an equilibrium value of  $\frac{E}{R}$  according to

$$i = \frac{E}{R} \left( 1 - e^{\frac{-t}{\tau_L}} \right)$$

Here  $\tau_L$ , the **inductive time constant**, is given by


$$\tau_L = \frac{L}{R}$$


#### **30-6 RL Circuits**

Plot (a) and (b) shows how the potential differences  $V_R (= iR)$  across the resistor and  $V_L \left(= L \frac{di}{dt}\right)$  across the inductor vary with

time for particular values of  $\exists$ , L, and R.

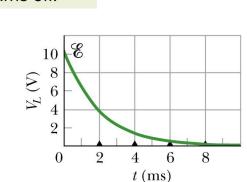The resistor's potential difference turns on.
The inductor's potential difference turns off.



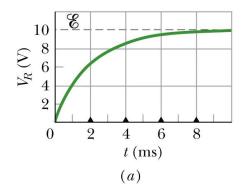

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

When the source of constant e m f is removed and replaced by a conductor, the **current decays** from a value  $i_0$  according to:  $E = \frac{-t}{\tau_c} = \frac{-t}{\tau_c}$ 


$$i = \frac{E}{R} e^{\frac{i}{\tau_L}} = i_0 e^{\frac{i}{\tau_L}}$$

(b)


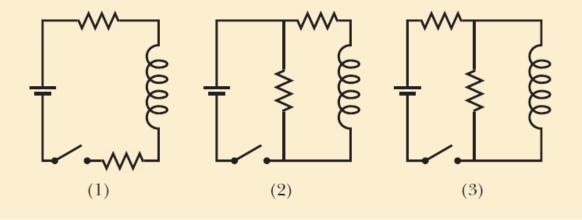
### Checkpoint 6

The figure shows three circuits with identical batteries, inductors, and resistors. Rank the circuits according to the current through the battery (a) just after the switch is closed and (b) a long time later, greatest first. (If you have trouble here, work through the next sample problem and then try again.)




(a) 
$$2, 3, 1$$
 (zero); (b)  $2, 3, 1$ 

# **30-7 Energy Stored in a Magnetic Field**

If an inductor L carries a current i, the inductor's magnetic field stores an energy given by

$$U_B = \frac{1}{2}Li^2$$

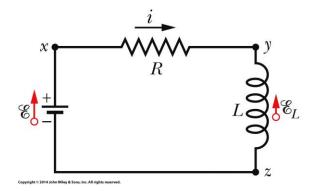

An RL circuit.

#### Sample Problem 30.06 RL circuit, current during the transition

A solenoid has an inductance of 53 mH and a resistance of 0.37  $\Omega$ . If the solenoid is connected to a battery, how long will the current take to reach half its final equilibrium value? (This is a *real solenoid* because we are considering its small, but nonzero, internal resistance.)

#### **KEY IDEA**

We can mentally separate the solenoid into a resistance and an inductance that are wired in series with a battery, as in Fig. 30-16. Then application of the loop rule leads to Eq. 30-39, which has the solution of Eq. 30-41 for the current *i* in the circuit.

**Calculations:** According to that solution, current i increases exponentially from zero to its final equilibrium value of  $\mathscr{C}/R$ . Let  $t_0$  be the time that current i takes to reach half its equilibrium value. Then Eq. 30-41 gives us

$$\frac{1}{2} \frac{\mathscr{E}}{R} = \frac{\mathscr{E}}{R} (1 - e^{-t_0/\tau_L}).$$

We solve for  $t_0$  by canceling  $\mathscr{E}/R$ , isolating the exponential, and taking the natural logarithm of each side. We find

$$t_0 = \tau_L \ln 2 = \frac{L}{R} \ln 2 = \frac{53 \times 10^{-3} \text{ H}}{0.37 \Omega} \ln 2$$
  
= 0.10 s. (Answer)

#### Sample Problem 30.07 Energy stored in a magnetic field

A coil has an inductance of 53 mH and a resistance of  $0.35\,\Omega$ .

(a) If a 12 V emf is applied across the coil, how much energy is stored in the magnetic field after the current has built up to its equilibrium value?

#### **KEY IDEA**

The energy stored in the magnetic field of a coil at any time depends on the current through the coil at that time, according to Eq. 30-49 ( $U_B = \frac{1}{2}Li^2$ ).

**Calculations:** Thus, to find the energy  $U_{B\infty}$  stored at equilibrium, we must first find the equilibrium current. From Eq. 30-41, the equilibrium current is

$$i_{\infty} = \frac{\mathscr{E}}{R} = \frac{12 \text{ V}}{0.35 \Omega} = 34.3 \text{ A}.$$
 (30-51)

Then substitution yields

$$U_{B\infty} = \frac{1}{2}Li_{\infty}^2 = (\frac{1}{2})(53 \times 10^{-3} \text{ H})(34.3 \text{ A})^2$$
  
= 31 J. (Answer)

(b) After how many time constants will half this equilibrium energy be stored in the magnetic field?

**Calculations:** Now we are being asked: At what time *t* will the relation

$$U_B = \frac{1}{2} U_{B\infty}$$

be satisfied? Using Eq. 30-49 twice allows us to rewrite this energy condition as

$$\frac{1}{2}Li^2 = (\frac{1}{2})\frac{1}{2}Li_{\infty}^2$$

or

$$i = \left(\frac{1}{\sqrt{2}}\right)i_{\infty}.\tag{30-52}$$

This equation tells us that, as the current increases from its initial value of 0 to its final value of  $i_{\infty}$ , the magnetic field will have half its final stored energy when the current has increased to this value. In general, we know that i is given by Eq. 30-41, and here  $i_{\infty}$  (see Eq. 30-51) is  $\mathscr{E}/R$ ; so Eq. 30-52 becomes

$$\frac{\mathscr{E}}{R}\left(1-e^{-t/\tau_L}\right)=\frac{\mathscr{E}}{\sqrt{2}R}.$$

By canceling  $\mathscr{E}/R$  and rearranging, we can write this as

$$e^{-t/\tau_L} = 1 - \frac{1}{\sqrt{2}} = 0.293,$$

which yields

$$\frac{t}{\tau_L} = -\ln 0.293 = 1.23$$

or

$$t \approx 1.2\tau_L$$
. (Answer)

Thus, the energy stored in the magnetic field of the coil by the current will reach half its equilibrium value 1.2 time constants after the emf is applied.