

CH31: Electromagnetic Oscillations and Alternating Current Lecture 5


Of the three circuit elements, resistance R, capacitance C, and inductance L, we have so far discussed the series combinations RC (in Module CH 27-4) and RL (in Module CH 30-6). In these two kinds of circuit we found that the charge, current, and potential difference grow and decay exponentially. The time scale of the growth or decay is given by a time constant t, which is either capacitive or inductive.

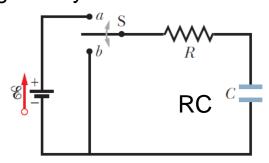

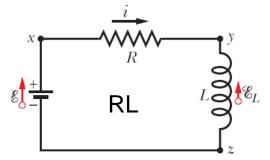


 $\tau = RC$ (time constant).
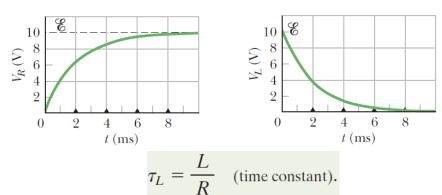
$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$
 (discharging a capacitor).



$$i = \frac{\mathscr{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$
 (decay of current).

Eight stages in a single cycle of oscillation of a resistance less LC circuit. The bar graphs by each figure show the stored magnetic and electrical energies. The magnetic field lines of the inductor and the electric field lines of the capacitor are shown. (a) Capacitor with maximum charge, no current. (b) Capacitor discharging, current increasing. (c) Capacitor fully discharged, current maximum. (d) Capacitor charging but with polarity opposite that in (a), current decreasing.

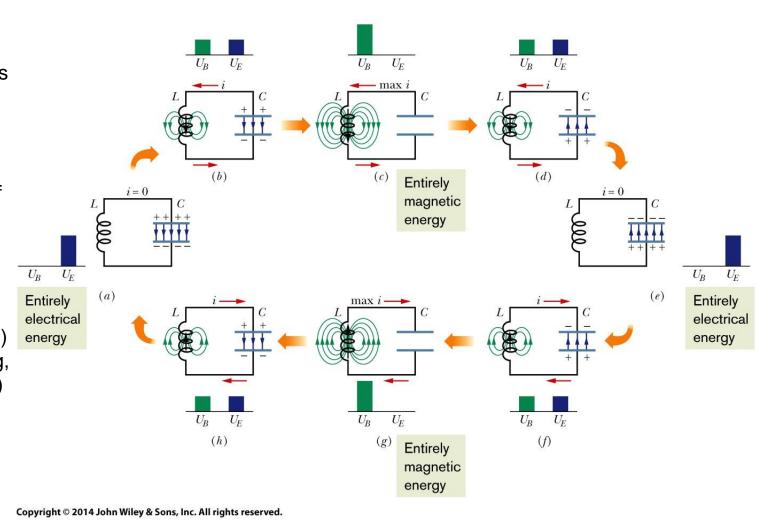

(e) Capacitor with maximum charge having polarity opposite that in (a), no current. (f) Capacitor discharging, current increasing with direction opposite that in (b). (g) Capacitor fully discharged, current maximum. (h) Capacitor charging, current decreasing.

Parts (a) through (h) of the Figure show succeeding stages of the oscillations in a simple LC circuit. The energy stored in the electric field of the **capacitor** at any time is $U_E = \frac{q^2}{2C}$

where *q* is the charge on the capacitor at that time. The energy stored in the magnetic field of the **inductor** at any time is

$$U_B = \frac{Li^2}{2}$$

where *i* is the current through the inductor at that time.

The resulting oscillations of the capacitor's electric field and the inductor's magnetic field are said to be **electromagnetic oscillations**.

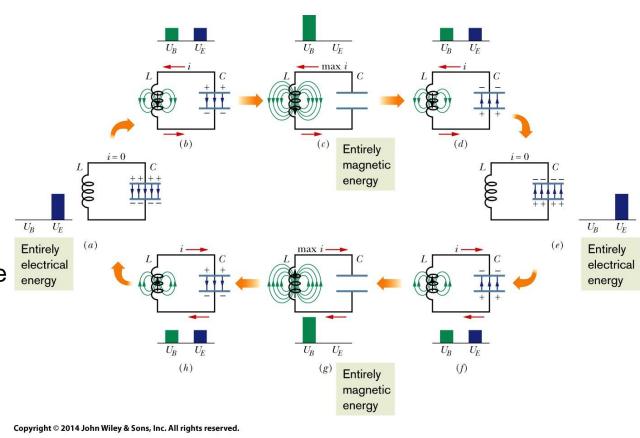


Table 31-1 Comparison of the Energy in Two Oscillating Systems

Block-Spring System		LC Oscillator		
Element	Energy	Element	Energy	
Spring	Potential, $\frac{1}{2}kx^2$	Capacitor	Electrical, $\frac{1}{2}(1/C)q^2$	
Block	Kinetic, $\frac{1}{2}mv^2$	Inductor	Magnetic, $\frac{1}{2}Li^2$	
v = dx/dt			i = dq/dt	

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

From the table we can deduce the correspondence between these systems. Thus,

q corresponds to x, 1/C corresponds to k, i corresponds to v, and L corresponds to m.

The correspondences listed above suggest that to find the angular frequency of oscillation for an ideal (resistanceless) LC circuit, k should be replaced by 1/C and m by L, yielding

$$\omega = \frac{1}{\sqrt{LC}} \quad (LC \, \text{circuit}).$$

LC Oscillator

The total energy U present at any instant in an oscillating LC circuit is given by

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

in which U_B is the energy stored in the magnetic field of the inductor and U_E is the energy stored in the electric field of the capacitor. Since we have assumed the circuit resistance to be zero, no energy is transferred to thermal energy and U remains constant with time. In more formal language, dU/dt must be zero. This leads to

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0.$$

However, i = dq/dt and $di/dt = d^2q/dt^2$. With these substitutions, we get

$$L\frac{d^2q}{dt^2} + \frac{1}{C}q = 0$$

This is the **differential equation** that describes the oscillations of a resistanceless LC circuit.

Charge and Current Oscillation

The solution for the differential equation equation that describes the oscillations of a resistanceless LC circuit is

$$q = Q\cos(\omega t + \phi)$$

where Q is the amplitude of the charge variations, ω is the angular frequency of the electromagnetic oscillations, and ϕ is the phase constant. Taking the first derivative of the above Eq. with respect to time gives us the current:

$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$

Checkpoint 2

A capacitor in an LC oscillator has a maximum potential difference of 17 V and a maximum energy of 160 μ J. When the capacitor has a potential difference of 5 V and an energy of 10 μ J, what are (a) the emf across the inductor and (b) the energy stored in the magnetic field?

Answer: (a)
$$\varepsilon_L = 12 \text{ V}$$

(b) $U_B = 150 \text{ µJ}$

Electrical and Magnetic Energy Oscillations

The electrical energy stored in the LC circuit at time t is,

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi).$$

The magnetic energy is,

$$U_B = \frac{Q^2}{2C}\sin^2(\omega t + \phi).$$

Figure shows plots of U_E (t) and U_B (t) for the case of $\phi = 0$. Note that


- 1. The maximum values of U_E and U_B are both $Q^2/2C$.
- 2. At any instant the sum of U_E and U_B is equal to $Q^2/2C$, a constant.
- 3. When U_E is maximum, U_B is zero, and conversely.



A charged capacitor and an inductor are connected in series at time t=0. In terms of the period T of the resulting oscillations, determine how much later the following reach their maximum value: (a) the charge on the capacitor; (b) the voltage across the capacitor, with its original polarity; (c) the energy stored in the electric field; and (d) the current.

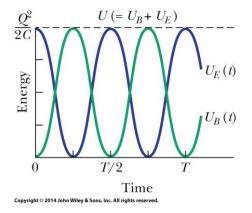(a)
$$T/2$$
; (b) T ; (c) $T/2$; (d) $T/4$

The electrical and magnetic energies vary but the total is constant.



The stored magnetic energy and electrical energy in the LC circuit as a function of time.

Sample Problem 31.01 LC oscillator: potential change, rate of current change

A 1.5 μ F capacitor is charged to 57 V by a battery, which is then removed. At time t=0, a 12 mH coil is connected in series with the capacitor to form an LC oscillator (Fig. 31-1).

(a) What is the potential difference $v_L(t)$ across the inductor as a function of time?

KEY IDEAS

(1) The current and potential differences of the circuit (both the potential difference of the capacitor and the potential difference of the coil) undergo sinusoidal oscillations. (2) We can still apply the loop rule to these oscillating potential differences, just as we did for the nonoscillating circuits of Chapter 27.


Calculations: At any time *t* during the oscillations, the loop rule and Fig. 31-1 give us

$$v_L(t) = v_C(t);$$
 (31-18)

that is, the potential difference v_L across the inductor must always be equal to the potential difference v_C across the capacitor, so that the net potential difference around the circuit is zero. Thus, we will find $v_L(t)$ if we can find $v_C(t)$, and we can find $v_C(t)$ from q(t) with Eq. 25-1 (q = CV).

Because the potential difference $v_C(t)$ is maximum when the oscillations begin at time t=0, the charge q on the capacitor must also be maximum then. Thus, phase constant ϕ must be zero; so Eq. 31-12 gives us

$$q = Q\cos\omega t. \tag{31-19}$$

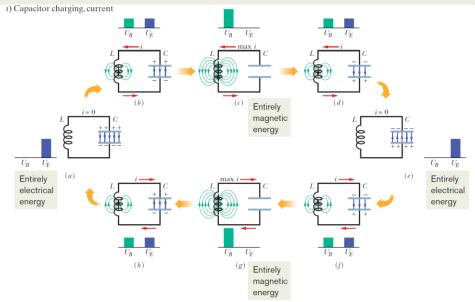

(Note that this cosine function does indeed yield maximum q (= Q) when t = 0.) To get the potential difference $v_C(t)$, we divide both sides of Eq. 31-19 by C to write

$$\frac{q}{C} = \frac{Q}{C}\cos\omega t,$$

and then use Eq. 25-1 to write

$$v_C = V_C \cos \omega t. \tag{31-20}$$

Here, V_C is the amplitude of the oscillations in the potential difference v_C across the capacitor.

Next, substituting $v_C = v_L$ from Eq. 31-18, we find

$$v_L = V_C \cos \omega t. \tag{31-21}$$

We can evaluate the right side of this equation by first noting that the amplitude V_C is equal to the initial (maximum) potential difference of 57 V across the capacitor. Then we find ω with Eq. 31-4:

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{[(0.012 \text{ H})(1.5 \times 10^{-6} \text{ F})]^{0.5}}$$
$$= 7454 \text{ rad/s} \approx 7500 \text{ rad/s}.$$

Thus, Eq. 31-21 becomes

$$v_L = (57 \text{ V}) \cos(7500 \text{ rad/s})t. \qquad (\text{Answer})$$

(b) What is the maximum rate $(di/dt)_{max}$ at which the current *i* changes in the circuit?

KEY IDEA

With the charge on the capacitor oscillating as in Eq. 31-12, the current is in the form of Eq. 31-13. Because $\phi = 0$, that equation gives us

$$i = -\omega Q \sin \omega t$$
.

Calculations: Taking the derivative, we have

$$\frac{di}{dt} = \frac{d}{dt} \left(-\omega Q \sin \omega t \right) = -\omega^2 Q \cos \omega t.$$

We can simplify this equation by substituting CV_C for Q (because we know C and V_C but not Q) and $1/\sqrt{LC}$ for ω according to Eq. 31-4. We get

$$\frac{di}{dt} = -\frac{1}{LC} CV_C \cos \omega t = -\frac{V_C}{L} \cos \omega t.$$

This tells us that the current changes at a varying (sinusoidal) rate, with its maximum rate of change being

$$\frac{V_C}{L} = \frac{57 \text{ V}}{0.012 \text{ H}} = 4750 \text{ A/s} \approx 4800 \text{ A/s}.$$
 (Answer)

31-2 Damped Oscillation in an RLC circuit

To analyze the oscillations of this circuit, we write an equation for the total electromagnetic energy U in the circuit at any instant. Because the resistance does not store electromagnetic energy, we can write

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}.$$


Now, however, this total energy decreases as energy is transferred to thermal energy. The rate of that transfer is,

$$\frac{dU}{dt}=-i^2R,$$

where the minus sign indicates that U decreases. By differentiating U with respect to time and then substituting the result we eventually get, $L\frac{d^2q}{dt^2} + R\frac{dq}{dt} + \frac{1}{C}q = 0$

which is the differential equation for **damped oscillations** in an RLC circuit.

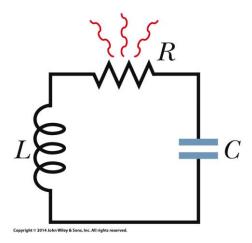Charge Decay. The solution to above Eq. is in which $\omega' = \sqrt{\omega^2 - (R/2L)^2}$ and $\omega = 1/\sqrt{LC}$,



A series RLC circuit. As the charge contained in the circuit oscillates back and forth through the resistance, electromagnetic energy is dissipated as thermal energy, damping (decreasing the amplitude of) the oscillations.

 $q = Qe^{-Rt/2L}\cos(\omega't + \phi)$

Sample Problem 31.02 Damped RLC circuit: charge amplitude

A series RLC circuit has inductance L=12 mH, capacitance C=1.6 μF , and resistance R=1.5 Ω and begins to oscillate at time t=0.

(a) At what time t will the amplitude of the charge oscillations in the circuit be 50% of its initial value? (Note that we do not know that initial value.)

KEY IDEA

The amplitude of the charge oscillations decreases exponentially with time t: According to Eq. 31-25, the charge amplitude at any time t is $Qe^{-Rt/2L}$, in which Q is the amplitude at time t = 0.

Calculations: We want the time when the charge amplitude has decreased to 0.50Q— that is, when

$$Qe^{-Rt/2L} = 0.50Q.$$

We can now cancel Q (which also means that we can answer the question without knowing the initial charge). Taking the natural logarithms of both sides (to eliminate the exponential function), we have

$$-\frac{Rt}{2L} = \ln 0.50.$$

Solving for *t* and then substituting given data yield

$$t = -\frac{2L}{R} \ln 0.50 = -\frac{(2)(12 \times 10^{-3} \text{ H})(\ln 0.50)}{1.5 \Omega}$$

= 0.0111 s \approx 11 ms. (Answer)

(b) How many oscillations are completed within this time?

KEY IDEA

The time for one complete oscillation is the period $T = 2\pi/\omega$, where the angular frequency for LC oscillations is given by Eq. 31-4 ($\omega = 1/\sqrt{LC}$).

Calculation: In the time interval $\Delta t = 0.0111$ s, the number of complete oscillations is

$$\frac{\Delta t}{T} = \frac{\Delta t}{2\pi\sqrt{LC}}$$

$$= \frac{0.0111 \text{ s}}{2\pi[(12 \times 10^{-3} \text{ H})(1.6 \times 10^{-6} \text{ F})]^{1/2}} \approx 13.$$
(Answer)

Thus, the amplitude decays by 50% in about 13 complete oscillations. This damping is less severe than that shown in Fig. 31-3, where the amplitude decays by a little more than 50% in one oscillation.