# CH31: Electromagnetic Oscillations and Alternating Current Lecture 6

# **31-3** Forced Oscillations of Three Simple Circuits


Why ac? The basic advantage of alternating current is this: As the current alternates, so does the magnetic field that surrounds the conductor. This makes possible the use of Faraday's law of induction, which, among other things, means that we can step up (increase) or step down (decrease) the magnitude of an alternating potential difference at will, using a device called a transformer, as we shall discuss later. Moreover, alternating current is more readily adaptable to rotating machinery such as generators and motors than is (nonalternating) direct current.
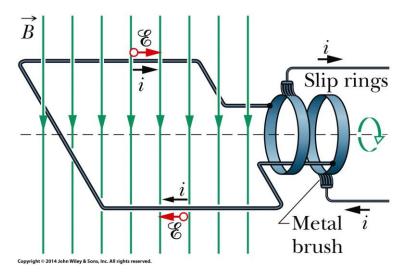
## **Forced Oscillations (with external emf)**



Whatever the natural angular frequency  $\omega$  of a circuit may be, forced oscillations of charge, current, and potential difference in the circuit always occur at the driving angular frequency  $\omega_d$ .

$$\mathscr{E} = \mathscr{E}_m \sin \omega_d t.$$
  
$$i = I \sin(\omega_d t - \phi),$$



The basic mechanism of an alternating-current generator is a conducting loop rotated in an external magnetic field. In practice, the alternating emf induced in a coil of many turns of wire is made accessible by means of slip rings attached to the rotating loop. Each ring is connected to one end of the loop wire and is electrically connected to the rest of the generator circuit by a conducting brush against which the ring slips as the loop (and ring) rotates.

# **31-3** Forced Oscillations of Three Simple

Circuits

# **Resistive Load**

The alternating potential difference across a resistor has amplitude

$$V_R = I_R R$$
 (resistor).


where  $V_R$  and  $I_R$  are the amplitudes of alternating current  $i_R$  and alternating potential difference  $v_R$  across the resistance in the circuit.

**Angular speed:** Both current and potential difference phasors rotate counterclockwise about the origin with an angular speed equal to the angular frequency  $\omega_d$  of  $\nu_R$  and  $i_R$ .

**Length**: The length of each phasor represents the amplitude of the alternating quantity:  $V_R$  for the voltage and  $I_R$  for the current.

**Projection**: The projection of each phasor on the vertical axis represents the value of the alternating quantity at time t.  $v_R$  for the voltage and  $i_R$  for the current.

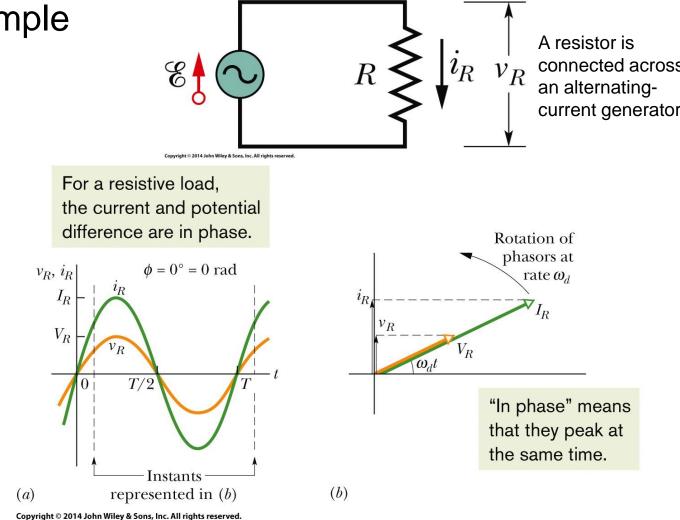**Rotation angle**: The rotation angle of each phasor is equal to the phase of the alternating quantity at time *t*.



(a) The current  $i_R$  and the potential difference  $v_R$  across the resistor are plotted on the same graph, both versus time t. They are in phase and complete one cycle in one period T. (b) A phasor diagram shows the same thing as (a).



If we increase the driving frequency in a circuit with a purely resistive load, do (a) amplitude  $V_R$  and (b) amplitude  $I_R$  increase, decrease, or remain the same?

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t.$$
  
$$i = I \sin(\omega_d t - \phi),$$

(a) remains the same; (b) remains the same

#### Sample Problem 31.03 Purely resistive load: potential difference and current

In Fig. 31-8, resistance R is 200  $\Omega$  and the sinusoidal alternating emf device operates at amplitude  $\mathcal{E}_m = 36.0 \text{ V}$  and frequency  $f_d = 60.0 \text{ Hz}$ .

(a) What is the potential difference  $v_R(t)$  across the resistance as a function of time t, and what is the amplitude  $V_R$  of  $v_R(t)$ ?

#### **KEY IDEA**

In a circuit with a purely resistive load, the potential difference  $v_R(t)$  across the resistance is always equal to the potential difference  $\mathscr{E}(t)$  across the emf device.

**Calculations:** For our situation,  $v_R(t) = \mathcal{E}(t)$  and  $V_R = \mathcal{E}_m$ . Since  $\mathcal{E}_m$  is given, we can write

$$V_R = \mathcal{E}_m = 36.0 \text{ V.} \tag{Answer}$$

To find  $v_R(t)$ , we use Eq. 31-28 to write

$$v_R(t) = \mathcal{E}(t) = \mathcal{E}_m \sin \omega_d t \tag{31-34}$$

and then substitute  $\mathscr{E}_m = 36.0 \text{ V}$  and

$$\omega_d = 2\pi f_d = 2\pi (60 \text{ Hz}) = 120\pi$$

to obtain

$$v_R = (36.0 \text{ V}) \sin(120\pi t).$$
 (Answer)

We can leave the argument of the sine in this form for convenience, or we can write it as (377 rad/s)t or as  $(377 \text{ s}^{-1})t$ .

(b) What are the current  $i_R(t)$  in the resistance and the amplitude  $I_R$  of  $i_R(t)$ ?

#### **KEY IDEA**

In an ac circuit with a purely resistive load, the alternating current  $i_R(t)$  in the resistance is *in phase* with the alternating potential difference  $v_R(t)$  across the resistance; that is, the phase constant  $\phi$  for the current is zero.

**Calculations:** Here we can write Eq. 31-29 as


$$i_R = I_R \sin(\omega_d t - \phi) = I_R \sin \omega_d t. \tag{31-35}$$

From Eq. 31-33, the amplitude  $I_R$  is

$$I_R = \frac{V_R}{R} = \frac{36.0 \text{ V}}{200 \Omega} = 0.180 \text{ A}.$$
 (Answer)

Substituting this and  $\omega_d = 2\pi f_d = 120\pi$  into Eq. 31-35, we have

$$i_R = (0.180 \text{ A}) \sin(120\pi t).$$
 (Answer)

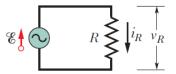

**Figure 31-8** A resistor is connected across an alternating-current generator.

# **31-3** Forced Oscillations of Three Simple Circuits

### **Inductive Load**

The **inductive reactance** of an inductor is defined as


$$X_L = \omega_d L$$


Its value depends not only on the inductance but also on the driving angular frequency  $\omega_{d^*}$  The voltage amplitude and current amplitude are related by

 $V_L = I_L X_L$ 

For an inductive load, the current lags the potential difference by 90°.

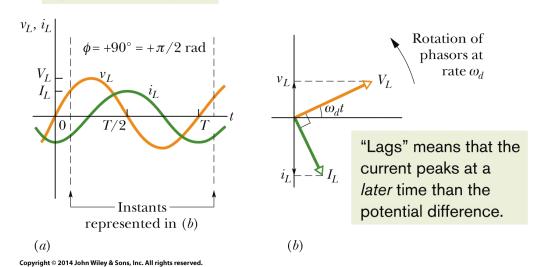(a)The current in the inductor lags the voltage by  $90^{\circ}$  ( =  $\pi/2$  rad). (b) A phasor diagram shows the same thing.



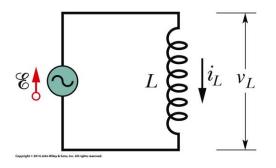

An inductor is connected across an alternating-current generator.

Fig. (left), shows that the quantities  $i_i$  and  $v_i$ are 90° out of phase. In this case, however,  $i_{i}$ lags  $v_i$ ; that is, monitoring the current  $i_{i}$ and the potential difference  $v_l$  in the circuit of Fig. (top) shows that  $i_l$  reaches its maximum value after  $\nu_{l}$  does, by one-quarter cycle.

#### Sample Problem 31.05 Purely inductive load: potential difference and current

In Fig. 31-12, inductance L is 230 mH and the sinusoidal alternating emf device operates at amplitude  $\mathcal{E}_m = 36.0 \text{ V}$  and frequency  $f_d = 60.0 \text{ Hz}$ .

(a) What are the potential difference  $v_L(t)$  across the inductance and the amplitude  $V_L$  of  $v_L(t)$ ?

#### **KEY IDEA**

In a circuit with a purely inductive load, the potential difference  $v_L(t)$  across the inductance is always equal to the potential difference  $\mathscr{E}(t)$  across the emf device.

**Calculations:** Here we have  $v_L(t) = \mathcal{E}(t)$  and  $V_L = \mathcal{E}_m$ . Since  $\mathcal{E}_m$  is given, we know that

$$V_L = \mathcal{E}_m = 36.0 \text{ V.} \qquad (\text{Answer})$$

To find  $v_L(t)$ , we use Eq. 31-28 to write

$$v_L(t) = \mathscr{E}(t) = \mathscr{E}_m \sin \omega_d t. \tag{31-53}$$

Then, substituting  $\mathscr{C}_m = 36.0 \text{ V}$  and  $\omega_d = 2\pi f_d = 120\pi$  into Eq. 31-53, we have

$$v_L = (36.0 \text{ V}) \sin(120\pi t).$$
 (Answer)

(b) What are the current  $i_L(t)$  in the circuit as a function of time and the amplitude  $I_L$  of  $i_L(t)$ ?

#### **KEY IDEA**

In an ac circuit with a purely inductive load, the alternating current  $i_L(t)$  in the inductance lags the alternating potential difference  $v_L(t)$  by 90°. (In the mnemonic of the problemsolving tactic, this circuit is "positively an ELI circuit," which tells us that the emf E leads the current I and that  $\phi$  is positive.)

**Calculations:** Because the phase constant  $\phi$  for the current is  $+90^{\circ}$ , or  $+\pi/2$  rad, we can write Eq. 31-29 as

$$i_L = I_L \sin(\omega_d t - \phi) = I_L \sin(\omega_d t - \pi/2). \tag{31-54}$$

We can find the amplitude  $I_L$  from Eq. 31-52 ( $V_L = I_L X_L$ ) if we first find the inductive reactance  $X_L$ . From Eq. 31-49 ( $X_L = \omega_d L$ ), with  $\omega_d = 2\pi f_d$ , we can write


$$X_L = 2\pi f_d L = (2\pi)(60.0 \text{ Hz})(230 \times 10^{-3} \text{ H})$$
  
= 86.7  $\Omega$ .

Then Eq. 31-52 tells us that the current amplitude is

$$I_L = \frac{V_L}{X_L} = \frac{36.0 \text{ V}}{86.7 \Omega} = 0.415 \text{ A}.$$
 (Answer)

Substituting this and  $\omega_d = 2\pi f_d = 120\pi$  into Eq. 31-54, we have

$$i_L = (0.415 \text{ A}) \sin(120\pi t - \pi/2).$$
 (Answer)

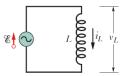

**Figure 31-12** An inductor is connected acros an alternating-current generator.

# 31-3 Forced Oscillations of Three Simple Circuits

# **Capacitive Load**


The **capacitive reactance** of a capacitor, defined as


$$X_C = \frac{1}{\omega_d C}$$

Its value depends not only on the capacitance but also on the driving angular frequency  $\omega_{d^*}$  The voltage amplitude and current amplitude are related by  $V_C = I_C X_C$ 

For a capacitive load, the current leads the potential difference by 90°.

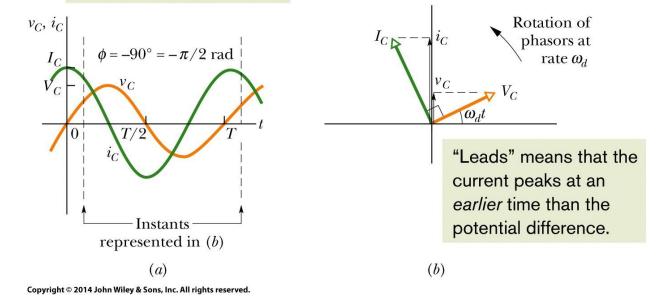(a)The current in the capacitor leads the voltage by 90° ( =  $\pi/2$  rad). (b) A phasor diagram shows the same thing.



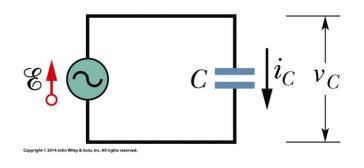

A capacitor is connected across an alternating-current generator.

In the phasor diagram we see that  $i_C$  leads  $v_C$ , which means that, if you monitored the current  $i_C$  and the potential difference  $v_C$  in the circuit above, you would find that  $i_C$  reaches its maximum before  $v_C$  does, by one-quarter cycle.

#### Sample Problem 31.04 Purely capacitive load: potential difference and current

In Fig. 31-10, capacitance C is 15.0  $\mu$ F and the sinusoidal alternating emf device operates at amplitude  $\mathcal{E}_m = 36.0 \text{ V}$  and frequency  $f_d = 60.0 \text{ Hz}$ .

(a) What are the potential difference  $v_C(t)$  across the capacitance and the amplitude  $V_C$  of  $v_C(t)$ ?

#### **KEY IDEA**

In a circuit with a purely capacitive load, the potential difference  $v_C(t)$  across the capacitance is always equal to the potential difference  $\mathscr{E}(t)$  across the emf device.

**Calculations:** Here we have  $v_C(t) = \mathcal{E}(t)$  and  $V_C = \mathcal{E}_m$ . Since  $\mathcal{E}_m$  is given, we have

$$V_C = \mathcal{E}_m = 36.0 \text{ V.} \tag{Answer}$$

To find  $v_C(t)$ , we use Eq. 31-28 to write

$$v_C(t) = \mathcal{E}(t) = \mathcal{E}_m \sin \omega_d t. \tag{31-43}$$

Then, substituting  $\mathscr{E}_m = 36.0 \text{ V}$  and  $\omega_d = 2\pi f_d = 120\pi$  into Eq. 31-43, we have

$$v_C = (36.0 \text{ V}) \sin(120\pi t).$$
 (Answer)

(b) What are the current  $i_C(t)$  in the circuit as a function of time and the amplitude  $I_C$  of  $i_C(t)$ ?

#### **KEY IDEA**

In an ac circuit with a purely capacitive load, the alternating current  $i_C(t)$  in the capacitance leads the alternating potential difference  $v_C(t)$  by 90°; that is, the phase constant  $\phi$  for the current is  $-90^\circ$ , or  $-\pi/2$  rad.

**Calculations:** Thus, we can write Eq. 31-29 as

$$i_C = I_C \sin(\omega_d t - \phi) = I_C \sin(\omega_d t + \pi/2). \tag{31-44}$$

We can find the amplitude  $I_C$  from Eq. 31-42 ( $V_C = I_C X_C$ ) if we first find the capacitive reactance  $X_C$ . From Eq. 31-39 ( $X_C = 1/\omega_d C$ ), with  $\omega_d = 2\pi f_d$ , we can write


$$X_C = \frac{1}{2\pi f_d C} = \frac{1}{(2\pi)(60.0 \text{ Hz})(15.0 \times 10^{-6} \text{ F})}$$
  
= 177  $\Omega$ .

Then Eq. 31-42 tells us that the current amplitude is

$$I_C = \frac{V_C}{X_C} = \frac{36.0 \text{ V}}{177 \Omega} = 0.203 \text{ A.}$$
 (Answer)

Substituting this and  $\omega_d = 2\pi f_d = 120\pi$  into Eq. 31-44, we have

$$i_C = (0.203 \text{ A}) \sin(120\pi t + \pi/2).$$
 (Answer)

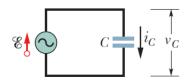

**Figure 31-10** A capacitor is connected across an alternating-current generator.



# **Checkpoint 5**

If we increase the driving frequency in a circuit with a purely capacitive load, do (a) amplitude  $V_C$  and (b) amplitude  $I_C$  increase, decrease, or remain the same? If, instead, the circuit has a purely inductive load, do (c) amplitude  $V_L$  and (d) amplitude  $I_L$  increase, decrease, or remain the same?

(a) remains the same; (b) increases;

(c) remains the same; (d) decreases

 $\mathscr{E} = \mathscr{E}_m \sin \omega_d t.$ 

 $i = I\sin(\omega_d t - \phi),$