King Fahd University of Petroleum and Minerals

College of Computing and Mathematics

Information and Computer Science Department

ICS 560: Foundation of Quantum Computing

Semester 251

Assignment 3

Show all necessary steps:

- 1. Compute (1 + 0|1 0).
- 2. Consider the two-qubit state

$$\frac{1}{4}|00\rangle + \frac{1}{2}|01\rangle + \frac{1}{\sqrt{2}}|10\rangle + \frac{\sqrt{3}}{4}|11\rangle.$$

If you measure only the left qubit, what are the resulting states, and with what probabilities?

3. Consider the three-qubit state

$$\frac{1}{6}|000\rangle + \frac{1}{3\sqrt{2}}|001\rangle + \frac{1}{\sqrt{6}}|010\rangle + \frac{1}{2}|011\rangle + \frac{1}{6}|100\rangle + \frac{1}{3}|101\rangle + \frac{1}{6}|110\rangle + \frac{1}{\sqrt{3}}|111\rangle.$$

If you measure only the left and right qubits, but not the middle qubit, what are the resulting states, and with what probabilities?

- 4. Are each of the following states seperable state or entangled state? If it is a product state, give the factorization.
 - a) $\frac{1}{\sqrt{2}}(|01\rangle |10\rangle)$
 - b) $\frac{1}{\sqrt{2}}(|10\rangle i|11\rangle)$
- 5. Are each of the following states a seperable state or entangled state? If it is a seperable state, give the factorization.

a)
$$\frac{1}{4}(3|00\rangle - \sqrt{3}|01\rangle + \sqrt{3}|10\rangle - |11\rangle)$$

b)
$$\frac{1}{\sqrt{3}}|0+\rangle + \sqrt{\frac{2}{3}}|1-\rangle$$

- 6. Prove the following circuit identities, such as by finding the matrix representation of each circuit.
 - a) $CNOT(I \otimes X) = (I \otimes X)CNOT$

$$= X$$


b) $CNOT(Z \otimes I) = (Z \otimes I)CNOT$

$$= \overline{Z}$$

- 7. The controlled-U (CU) gate applies some quantum gate U to the right qubit if the left qubit is 1. Write the controlled-Z and controlled-Y gates as a matrix
- 8. A unitary U that is able to clone qubits in two known state $|\psi\rangle$ That is, $U|\psi\rangle|0\rangle = |\psi\rangle|\psi\rangle$, Does there exist a quantum operator U that can clone both?
 - a) $|+\rangle$ and $|i\rangle$
 - b)

$$\frac{1+\sqrt{3}i}{4}|0\rangle+\frac{\sqrt{2}-i}{2}|1\rangle$$
 and $\frac{\sqrt{2}+i}{2}|0\rangle+\frac{-1+\sqrt{3}i}{4}|1\rangle$.

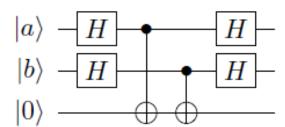9. Consider the following quantum circuit:



- a) If $|a\rangle = |-\rangle$ and $|b\rangle = |+\rangle$, find the resulting state at the end of the circuit.
- b) If $|a\rangle = |-\rangle$ and $|b\rangle = |-\rangle$, find the resulting state at the end of the circuit.